

CS M51A, Winter 2021, Assignment 5  
 (Total Mark: 110 points, 11% )

Due: Wed Feb 10th, 10:00 AM Pacific Time

Student Name:


Student ID:

**Note:** You must complete the assignments entirely on your own,  
 without discussing with others.

- Given the following table:

$x_2$	$x_1$	$x_0$	$F$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

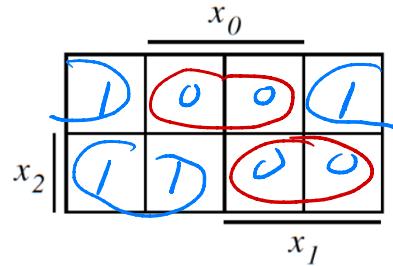- (4 points) Fill out the k-maps for this table.



- (4 points) Write the minimal sum of products for F.


$$\bar{F} = x_2' x_0' + x_2 x_1'$$

- (4 points) Write the minimal product of sums for F.

$$F = (x_0' + x_2)(x_1' + x_2')$$

2. Given  $f(x_3, x_2, x_1, x_0) = x_3x_2x_1x'_0 + x_3x_2x_1x_0 + x'_3x_2x'_1x_0 + x'_3x_2x_1x_0 + x_3x_2x'_1x'_0 + x_3x'_2x_1x_0 + x_3x'_2x_1x'_0$

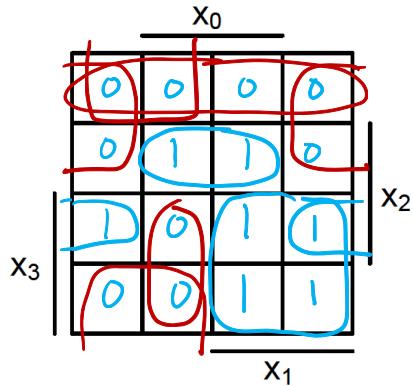(a) (8 points) Fill out the following K-maps.




(b) (4 points) Write the minimal sum of products expression for  $f$ .

$$f = x_3x_1 + x_3'x_2x_0 + x_3x_2x_0'$$


(c) (4 points) Write the minimal product of sums expression for  $f$ .

$$f = (x_3 + x_2)(x_3 + x_0)(x_2 + x_1)(x_2' + x_1 + x_0')$$

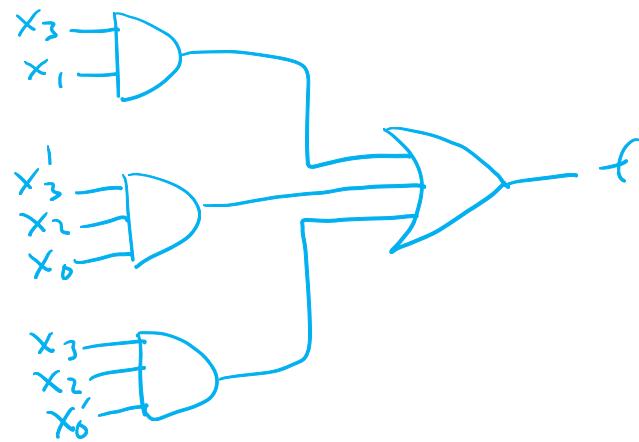(d) (4 points) Draw the gate level design for (b)



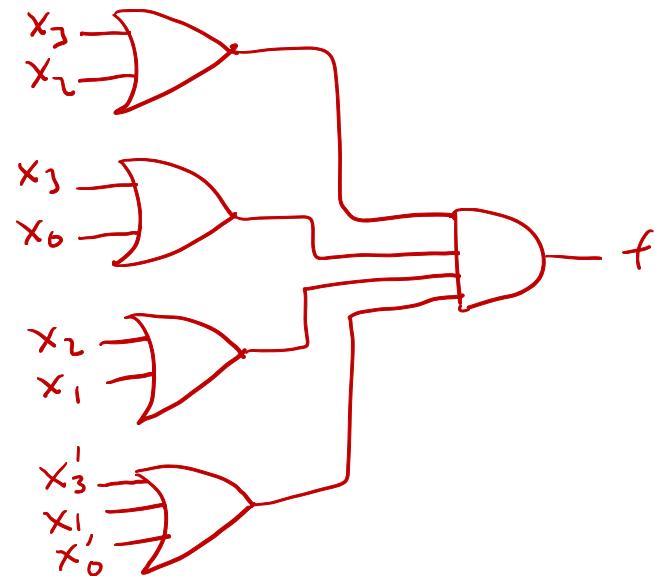(e) (4 points) Draw the gate level design for (c)




3. Consider a system that takes a decimal number (i.e. 0 to 9) as an input. The input is presented using a 4-bit unsigned binary code ( $x_3, x_2, x_1, x_0$ ). For example, if the input is 7,  $x_3 = 0, x_2 = 1, x_1 = 1, x_0 = 1$ . The system has a 2-bit output ( $z_1, z_0$ ).  $z_1$  is one when the input is an odd number, otherwise it is zero.  $z_0$  is one when the input is larger or equal to 5, otherwise it is zero.

(a) (8 points) Fill the truth table for this system.

$x_3$	$x_2$	$x_1$	$x_0$	$z_1$	$z_0$
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	1	1
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

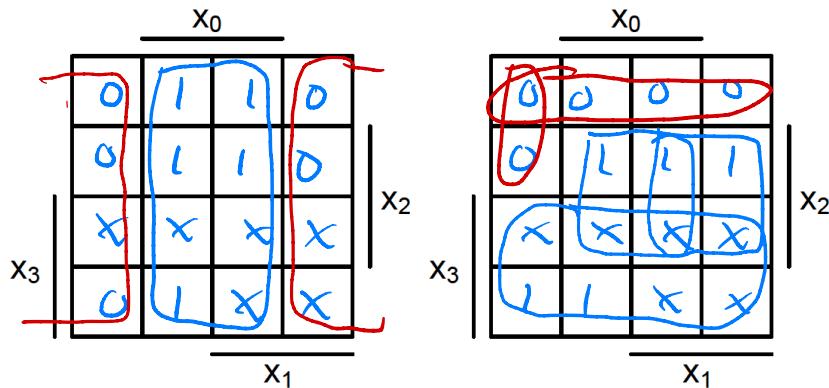(b) (4 points) Fill out the k-maps for this system (Left:  $z_1$ , Right:  $z_0$ ).



(c) (4 points) Write the minimal sum of products expression for the outputs (for both  $z_1$  and  $z_0$ ).

$$\Sigma_1 = X_0$$

$$\Sigma_0 = X_3 + X_0 X_2 + X_1 X_2$$


(d) (4 points) Write the minimal product of sums expression for the outputs (for both  $z_1$  and  $z_0$ ).

$$z_1 = x_0$$

$$z_0 = (x_3 + x_2)(x_3 + x_1 + x_0)$$


(e) (4 points) Draw a gate level design for (b) (for both  $z_1$  and  $z_0$ )

$$x_0 \rightarrow z_1$$

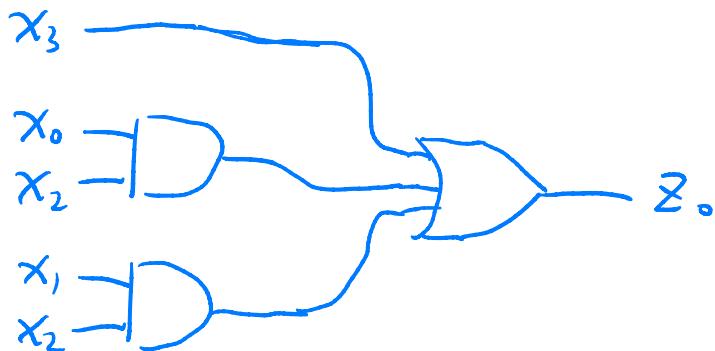

(f) (4 points) Draw a gate level design for (c) (for both  $z_1$  and  $z_0$ )


$$x_0 \rightarrow z_1$$

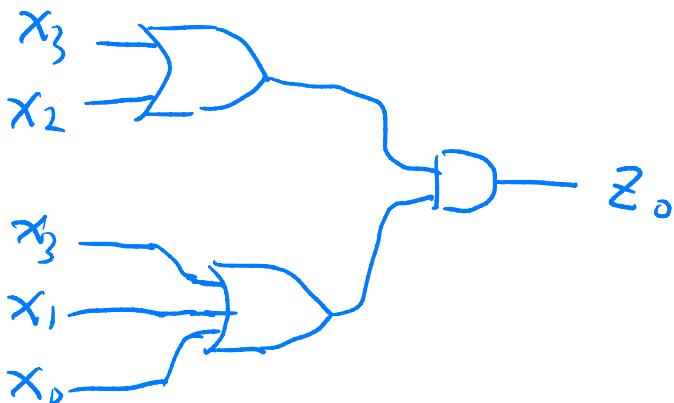

4. Using K-maps, find the minimal SOP and POS that are equivalent to the following expressions ( $dc(\dots)$  indicates the "don't care" terms):

(a) (5 Points)  $F(x_3, x_2, x_1, x_0) = \Pi M(1, 3, 4, 7, 10, 13, 14, 15)$  Maxterm = put 0

This can also be  
 $x_3'x_2'x_1'x_0'$

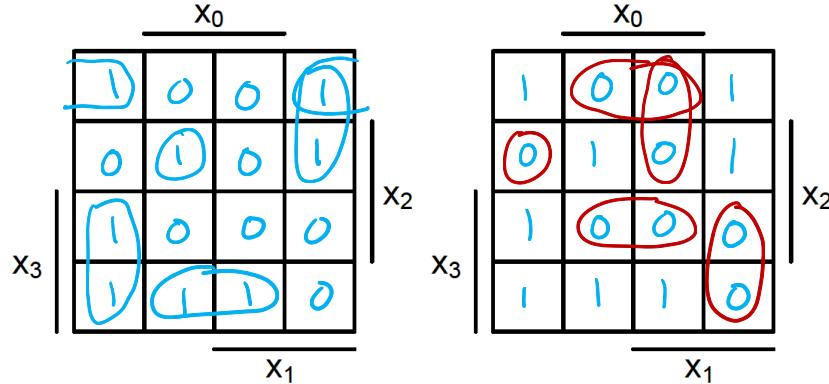


$$F = [x_3'x_2'x_1'x_0'] + x_3'x_2x_1'x_0' + x_3x_2'x_1'x_0' + x_3x_2'x_1x_0 + x_3'x_2x_1x_0 + x_3'x_2x_1'x_0$$

$$F = (x_3 + x_2 + x_0')(x_3 + x_2' + x_0)(x_3' + x_2 + x_0')(x_3' + x_2' + x_0)(x_3 + x_2' + x_1 + x_0)$$

(b) (5 Points)  $F(x_3, x_2, x_1, x_0) = \Sigma m(0, 4, 5, 9, 11, 14, 15), dc(x_3, x_2, x_1, x_0) = \{m(2), m(8)\}$

This can also be  
 $x_3'x_2'x_1'x_0'$

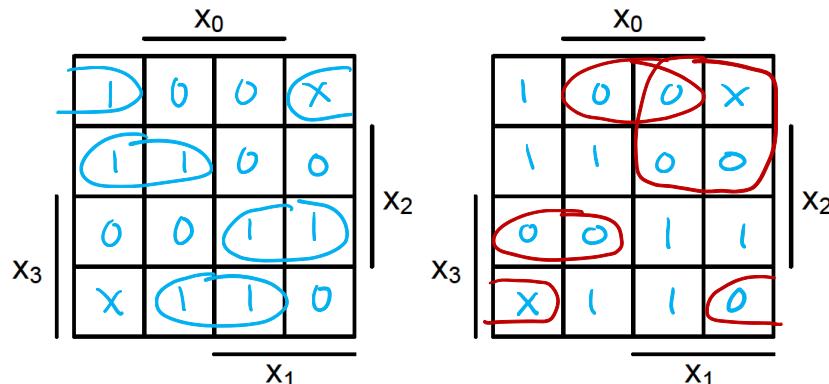


$$F = [x_3'x_2'x_1'x_0'] + x_3'x_2x_1' + x_3x_2x_1 + x_3x_2'x_0$$

$$F = (x_3' + x_2 + x_0)(x_3 + x_1')(x_3 + x_2 + x_0')(x_3' + x_2' + x_1)$$

This can also be

$$(x_2 + x_1' + x_0)$$

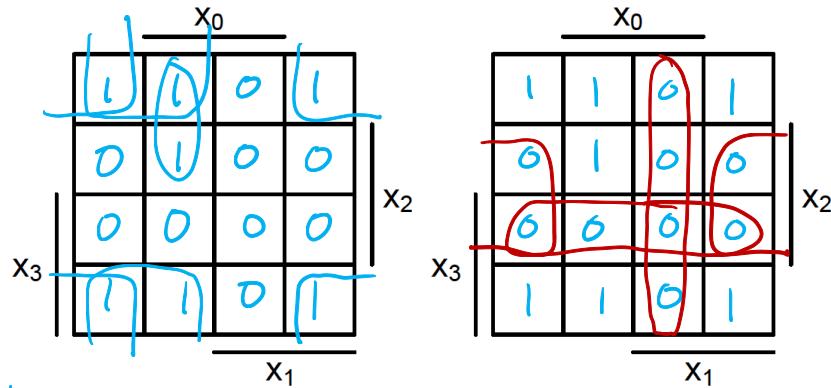
$$(c) \text{ (5 Points)} F(x_3, x_2, x_1, x_0) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$$



$$F = x_2'x_0' + x_1'x_1' + x_3'x_1'x_0'$$

$$F = (x_1' + x_0')(x_3' + x_2')(x_2' + x_0')$$
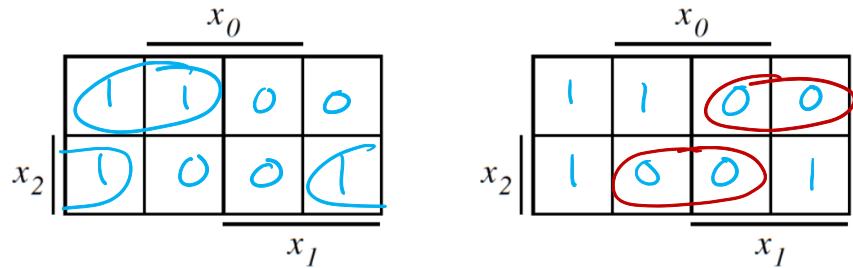
$$(d) \text{ (5 Points)} F(x_2, x_1, x_0) = \Sigma m(0, 1, 4, 6)$$




$$F = x_2'x_1' + x_2x_0'$$

$$F = (x_2 + x_1')(x_2' + x_0')$$

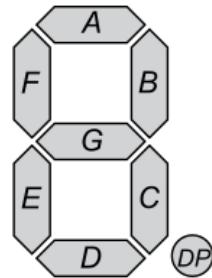5. Given the following (uncompleted) high-level specification:

Input:  $x \in \{0, 1, 2, \dots, 9\}$ , represented in unsigned binary code by 4 bits,  $x = (x_3, x_2, x_1, x_0)$ ;  
 Output:  $z \in \{0, 1\}$ .  $z$  is one bit and indicates whether the "G" segment of the 7-segment display below is illuminated when the displayed number is  $x$ . **For example:** the "G" segment is illuminated when  $x = 8$ , while it will be off when  $x = 0$ .



(a) (8 Points) Write the sum of minterms and product of maxterms of  $z$  given  $\{x_3, x_2, x_1, x_0\}$ .


"G" is illuminated when  $x = 2, 3, 4, 5, 6, 8, 9$

$$Z = \overline{\Sigma}m(2, 3, 4, 5, 6, 8, 9)$$

$$= \overline{\Pi}M(0, 1, 7)$$

$$dc(x_3, x_2, x_1, x_0) = \overline{\Sigma}m(10, 11, 12, 13, 14, 15)$$


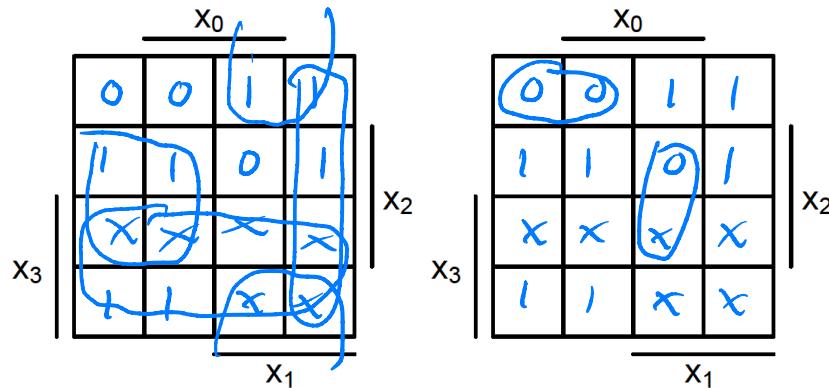
(b) (8 Points) Simplify the sum of minterms and product of maxterms in (a) using K-Map. (Hint: you may need to identify and utilize the "don't care" terms in this system)



$$Z = x_3 + x_2x_1' + x_1x_0' + x_2'x_1 \dots \text{Sop}$$

$$= (x_3 + x_2 + x_1)(x_2' + x_1' + x_0') \dots \text{Pos}$$

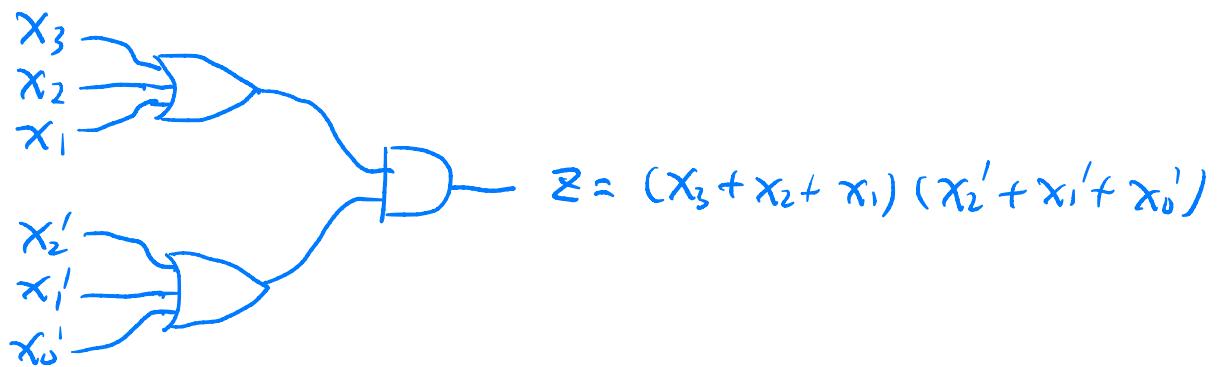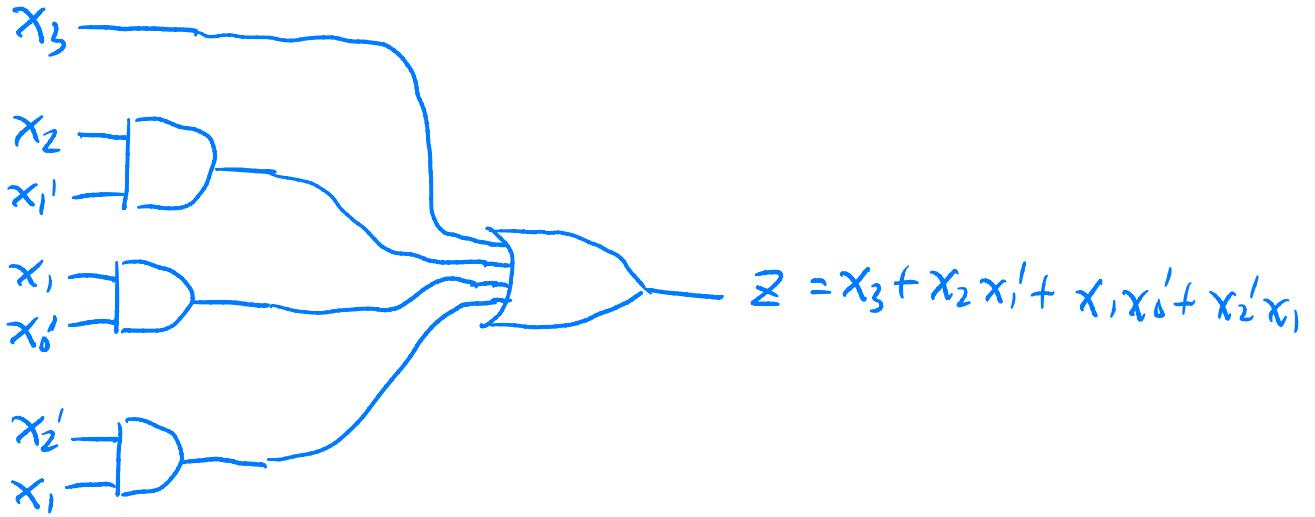(c) (8 points) Draw a gate level design for the minimal SOP and POS in (b)



6. (2 Points) What is an advantage of a NAND-NAND network over a AND-OR network?

NAND-NAND networks are made from NAND gates, which use less transistors than AND gates and OR gates.